
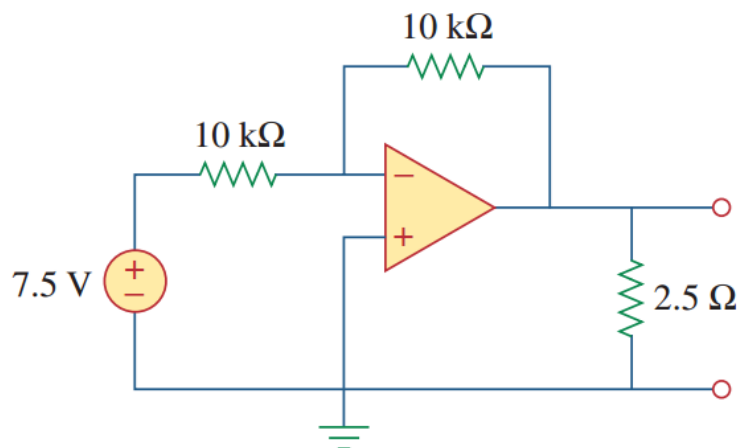


**\*5.18** For the circuit shown in Figure 5.57, solve for the Thevenin equivalent circuit looking into terminals A and B.

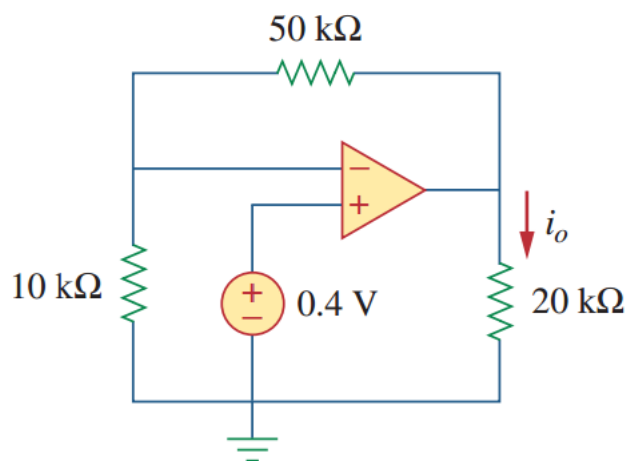


**Figure 5.57**  
For Prob. 5.18.

**5.28** Find  $i_o$  in the op amp circuit of Fig. 5.66.




**Figure 5.66**  
For Prob. 5.28.

**5.34** Given the op amp circuit shown in Fig. 5.72, express  $v_o$  in terms of  $v_1$  and  $v_2$ .

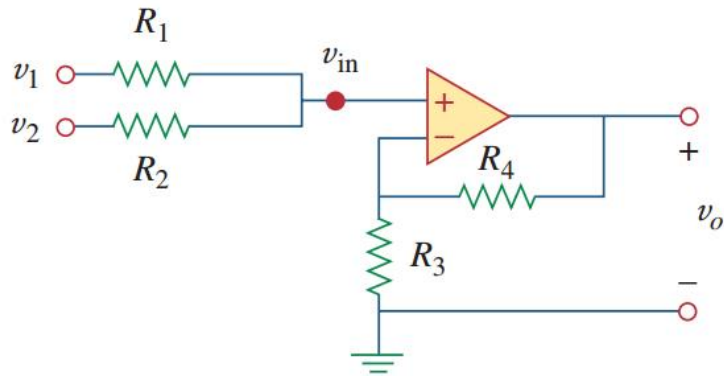

**Figure 5.72**  
For Prob. 5.34.

**5.37** Determine the output of the summing amplifier in Fig. 5.74.

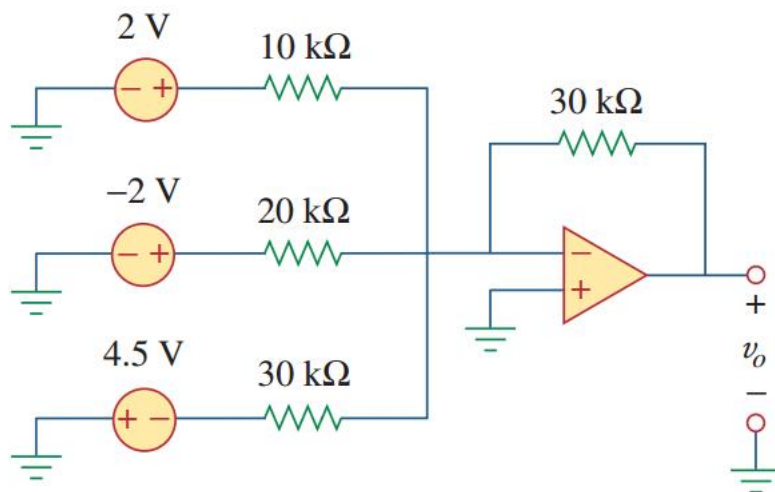


**Figure 5.74**  
For Prob. 5.37.

**5.46** Using only two op amps, design a circuit to solve

**end**

$$-v_{\text{out}} = \frac{v_1 - v_2}{3} + \frac{v_3}{2}$$

**5.61** Determine  $v_o$  in the circuit of Fig. 5.88.

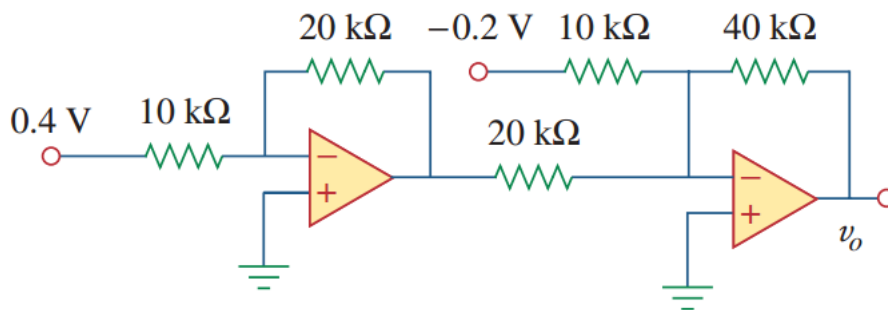


**Figure 5.88**

For Prob. 5.61.

**6.12** A voltage of  $30e^{-2000t}$  V appears across a parallel combination of a 100-mF capacitor and a 12-Ω resistor. Calculate the power absorbed by the parallel combination.

- 6.42** If the voltage waveform in Fig. 6.67 is applied across the terminals of a 5-H inductor, calculate the current through the inductor. Assume  $i(0) = -1$  A.

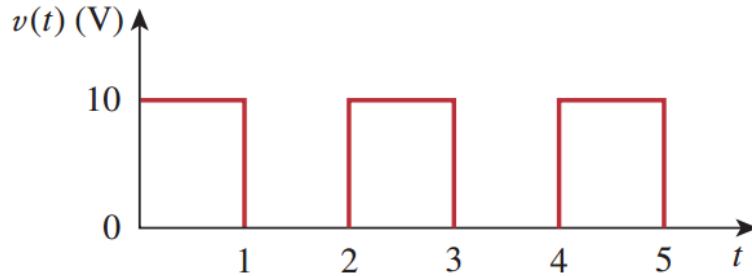

**Figure 6.67**

For Prob. 6.42.

- 6.66** The current  $i(t)$  through a 20-mH inductor is equal, in magnitude, to the voltage across it for all values of time. If  $i(0) = 2$  A, find  $i(t)$ .