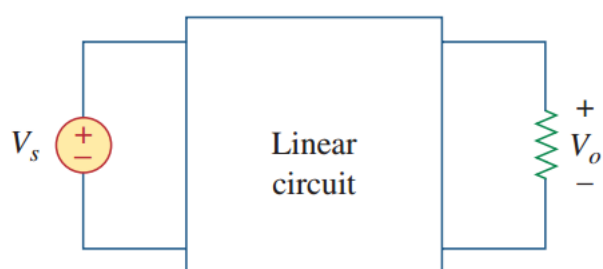



- 4.6** For the linear circuit shown in Fig. 4.74, use linearity to complete the following table.

Experiment	$V_s$	$V_o$
1	12 V	4 V
2		16 V
3	1 V	
4		-2 V




**Figure 4.74**  
For Prob. 4.6.

- 4.12** Determine  $v_o$  in the circuit of Fig. 4.80 using the superposition principle.

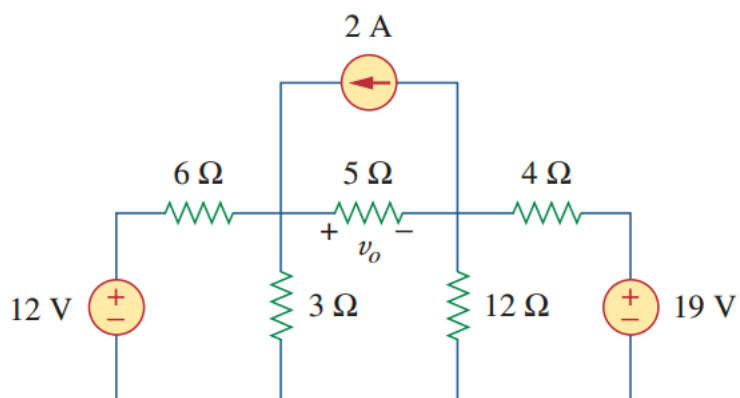

**Figure 4.80**  
For Prob. 4.12.


**4.22** For the circuit in Fig. 4.90, use source transformation to find  $i$ .

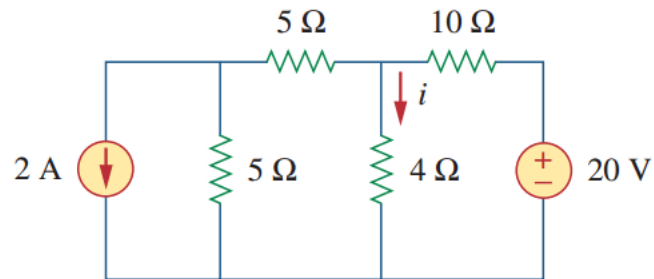

**Figure 4.90**

For Prob. 4.22.


**4.30** Use source transformation on the circuit shown in Fig 4.98 to find  $i_x$ .

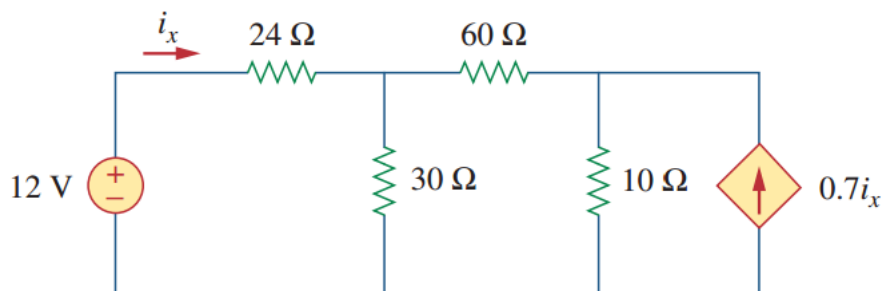

**Figure 4.98**

For Prob. 4.30.


- 4.34** Using Fig. 4.102, design a problem that will help other students better understand Thevenin equivalent circuits.

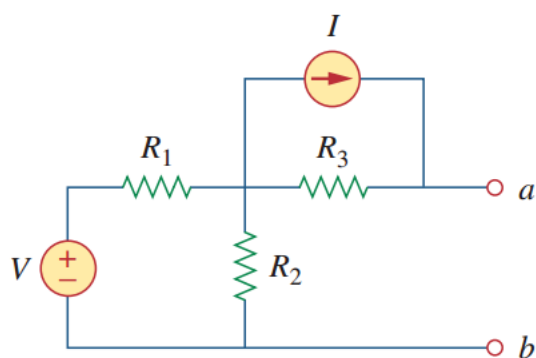

**Figure 4.102**

For Probs. 4.34 and 4.49.


- 4.52** For the transistor model in Fig. 4.118, obtain the Thevenin equivalent at terminals  $a$ - $b$ .

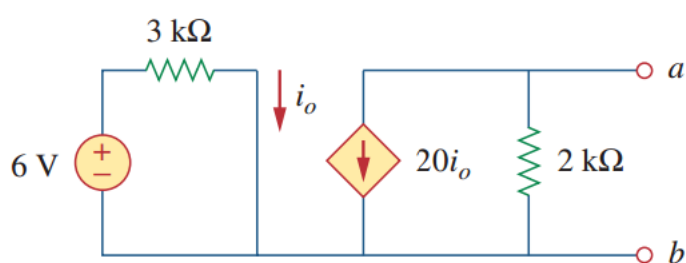

**Figure 4.118**

For Prob. 4.52.


**\*4.60** For the circuit in Fig. 4.126, find the Thevenin and Norton equivalent circuits at terminals  $a$ - $b$ .

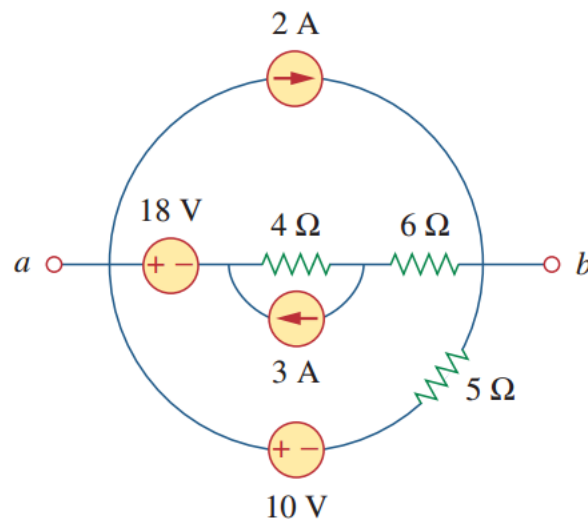

**Figure 4.126**

For Probs. 4.60 and 4.81.

**\*4.75** For the circuit in Fig. 4.141, determine the value of  $R$  such that the maximum power delivered to the load is 3 mW.

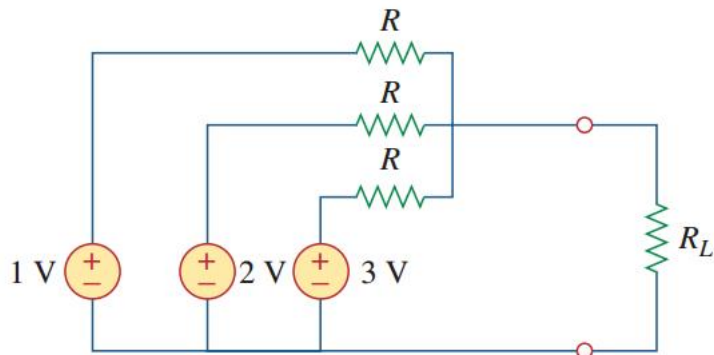

**Figure 4.141**

For Prob. 4.75.

**4.78** Use *PSpice* or *MultiSim* to solve Prob. 4.52.