

- 14.22** Find the transfer function $\mathbf{H}(\omega)$ with the Bode magnitude plot shown in Fig. 14.74.

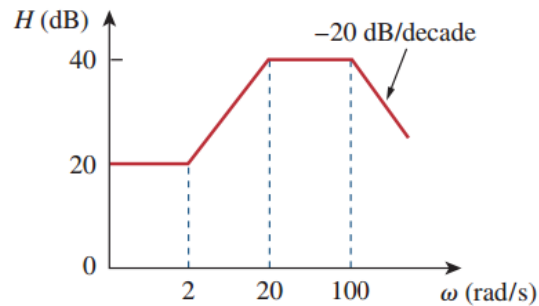


Figure 14.74
For Prob. 14.22.

- 14.25** A series RLC network has $R = 2 \text{ k}\Omega$, $L = 40 \text{ mH}$, and $C = 1 \text{ }\mu\text{F}$. Calculate the impedance at resonance and at one-fourth, one-half, twice, and four times the resonant frequency.

- 14.29** Let $v_s = 20 \cos(at) \text{ V}$ in the circuit of Fig. 14.77. Find ω_0 , Q , and B , as seen by the capacitor.

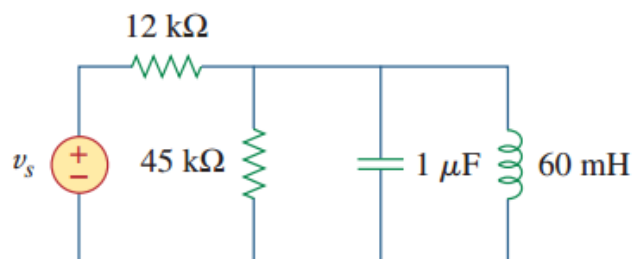


Figure 14.77
For Prob. 14.29.

***14.44** For the circuit in Fig. 14.83, find:

(a) the resonant frequency ω_0

(b) $Z_{in}(\omega_0)$

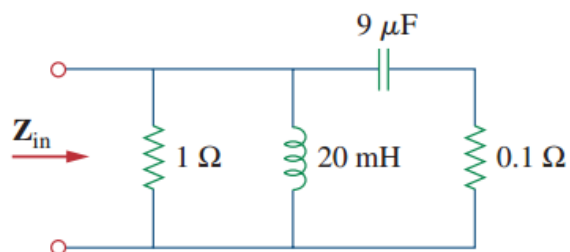


Figure 14.83

For Prob. 14.44.

14.50 Determine what type of filter is in Fig. 14.87.

Calculate the corner frequency f_c .

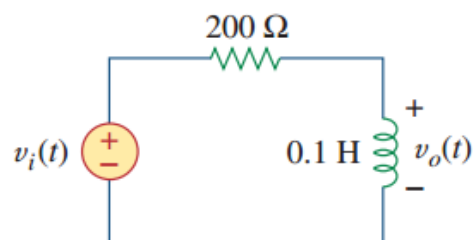


Figure 14.87

For Prob. 14.50.

- 14.64** Obtain the transfer function of the active filter in Fig. 14.91 on the next page. What kind of filter is it?

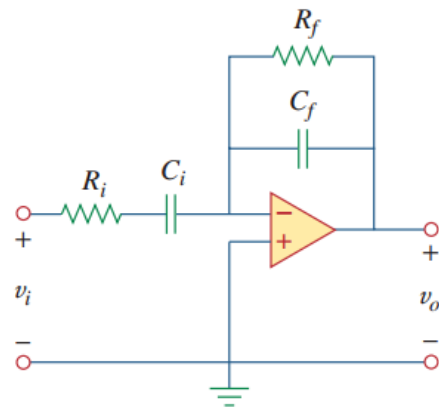


Figure 14.91
For Prob. 14.64.

- *14.70** A second-order active filter known as a Butterworth filter is shown in Fig. 14.95.



- (a) Find the transfer function V_o/V_i .
(b) Show that it is a lowpass filter.

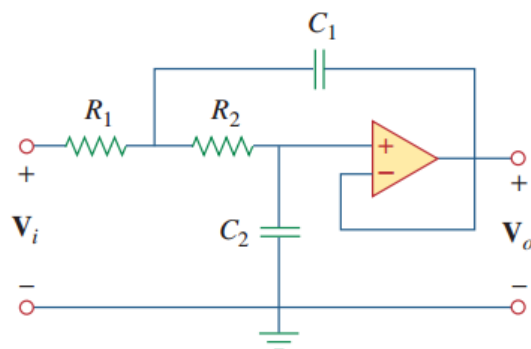


Figure 14.95
For Prob. 14.70.

- 14.84** Using *PSpice* or *MultiSim*, obtain the frequency response of the circuit in Fig. 14.101 on the next page.

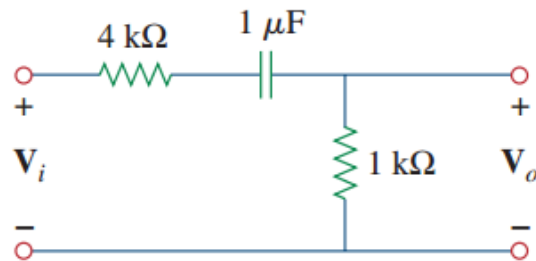


Figure 14.101
For Prob. 14.84.