

C4 Problems

For the circuit in Fig. 4.3, find v_o when $i_s = 30$ and $i_s = 45$ A.

Answer: 40 V, 60 V.

Practice Problem 4.1

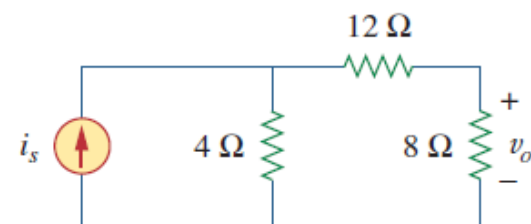


Figure 4.3

For Practice Prob. 4.1.

Practice Problem 4.2

Assume that $V_o = 1$ V and use linearity to calculate the actual value of V_o in the circuit of Fig. 4.5.

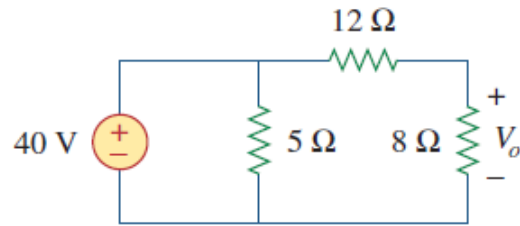


Figure 4.5

For Practice Prob. 4.2.

Answer: 16 V.

Practice Problem 4.3

Using the superposition theorem, find v_o in the circuit of Fig. 4.8.

Answer: 7.4 V.

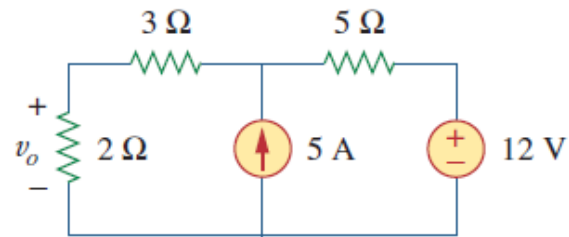


Figure 4.8

For Practice Prob. 4.3.

Find I in the circuit of Fig. 4.14 using the superposition principle.

Practice Problem 4.5

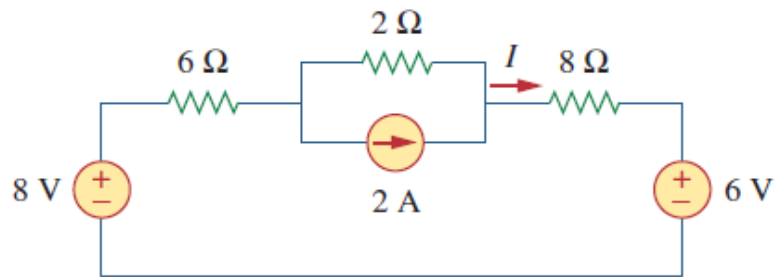


Figure 4.14

For Practice Prob. 4.5.

Answer: 375 mA.

Find i_o in the circuit of Fig. 4.19 using source transformation.

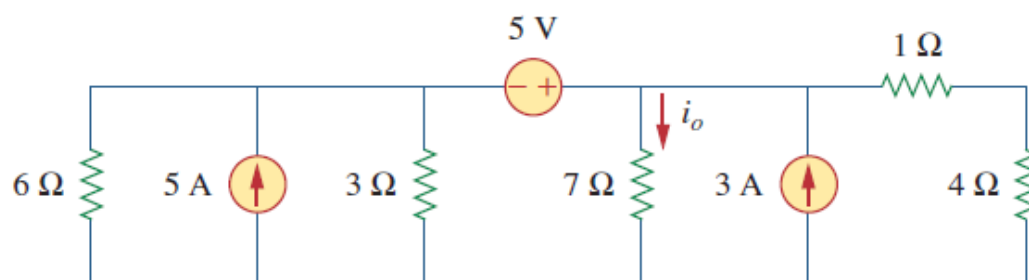


Figure 4.19

For Practice Prob. 4.6.

Answer: 1.78 A .

Practice Problem 4.8

Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit of Fig. 4.30. Then find I .

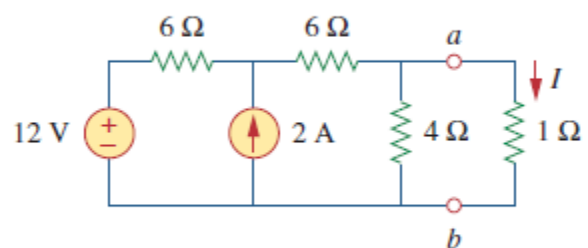


Figure 4.30

For Practice Prob. 4.8.

Answer: $V_{\text{Th}} = 6\text{ V}$, $R_{\text{Th}} = 3\ \Omega$, $I = 1.5\text{ A}$.

Obtain the Thevenin equivalent of the circuit in Fig. 4.36.

Practice Problem 4.10

Answer: $V_{\text{Th}} = 0 \text{ V}$, $R_{\text{Th}} = -7.5 \Omega$.

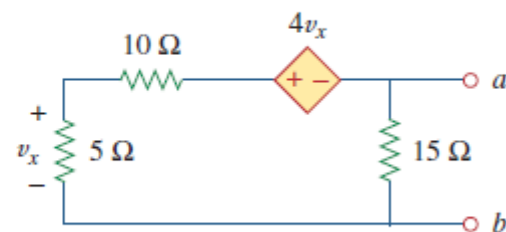


Figure 4.36

For Practice Prob. 4.10.

Practice Problem 4.12

Find the Norton equivalent circuit of the circuit in Fig. 4.45 at terminals a - b .

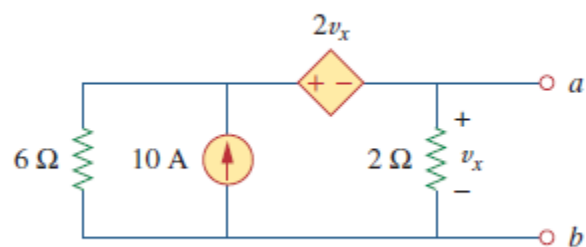


Figure 4.45

For Practice Prob. 4.12.

Answer: $R_N = 1\ \Omega$, $I_N = 10\text{ A}$.

Practice Problem 4.13

Determine the value of R_L that will draw the maximum power from the rest of the circuit in Fig. 4.52. Calculate the maximum power.

Answer: 4.222 Ω , 2.901 W.

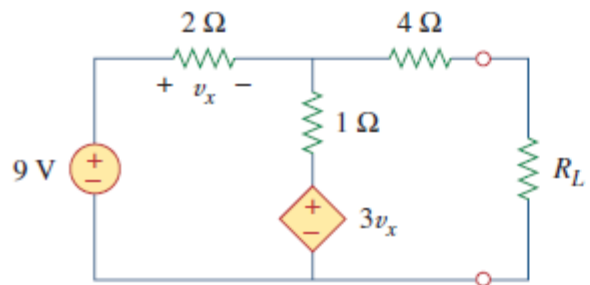


Figure 4.52

For Practice Prob. 4.13.

Practice Problem 4.16

The measured open-circuit voltage across a certain amplifier is 9 V. The voltage drops to 8 V when a $20\text{-}\Omega$ loudspeaker is connected to the amplifier. Calculate the voltage when a $10\text{-}\Omega$ loudspeaker is used instead.

Answer: 7.2 V.